

# **Reversible Gates**

Tags Part I SubUnit I

## **Circuits and Entropy**

- Classic gates destroy randomness → Consume energy!
- By Landauer's principle:


 $kT \ln 2$  energy needed per bit!

• Need reversible gates to preform low energy computing.

### **Reversible Gates**

1. **CNOT**: Controlled NOT


Reversible Gates 1

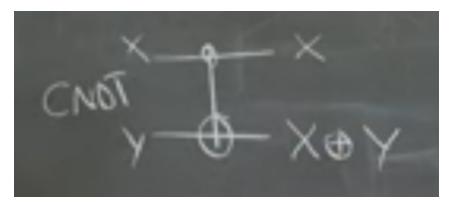

Controlled Not, if X is true, output is NOT Y. Otherwise, all stay the same.
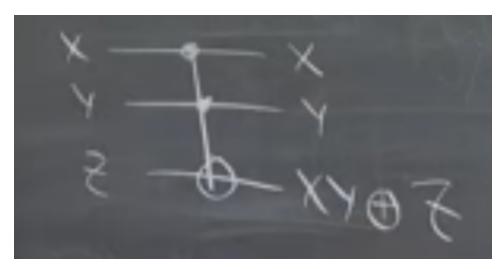
#### 2. Toffoli gate or CCNOT: Controlled Controlled NOT.

This gate is universal by itself, because it can simulate both AND and NOT gates.



If both X and Y are true, output is NOT Z. Otherwise, all stay the same.


### 3. Fredkin gate or CSWAP: Controlled Swap.

This gate is universal by itself, because it can simulate both AND and NOT gates.

If we set Y = 1 and Z = 0, it simulates the NOT gate!

Fredkin gate cannot change the Hamming weight (number of one's) of its inputs.

Reversible Gates 2

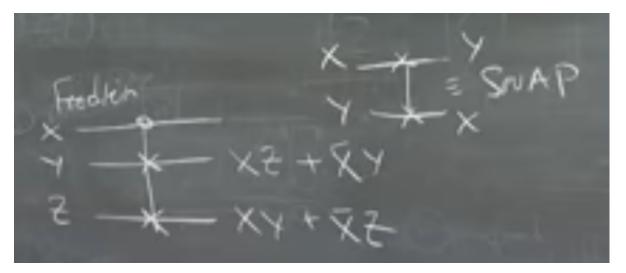

If X is true, Y and Z get swapped,. Otherwise, all stay the same.



**Theorem**: The number of garbage outputs in these gates to simulate a circuit is O(width of circuits).



**Theorem**: Any Boolean circuit of size n can be simulated by a reversible circuit of order of polynomial in n reversible gates. (approx. O(n^2))

**Def**.: "in-place reversible": No garbage bits are allowed, and no extra ancilla bits are provided (constant zero or one).

Reversible Gates 3